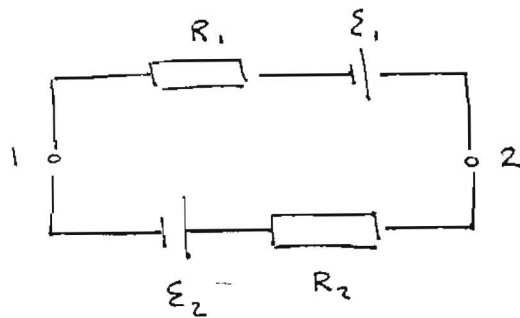


3.174)



$$R_1 = 10\Omega$$

$$R_2 = 20\Omega$$

$$E_1 = 5V$$

$$E_2 = 2V$$


find  $\phi_1 - \phi_2$  (potential difference between points 1 and 2)

from Kirchoff Loop

$$-E_1 + IR_1 + IR_2 + E_2 = 0$$

$$I = \frac{E_1 - E_2}{R_1 + R_2}$$

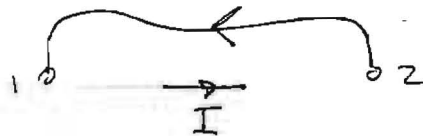
$\phi_1 - \phi_2$  draw path from 1  $\rightarrow$  2 and calculate drop across path



$$\Delta\phi = IR_1 - E_1 = \left( \frac{E_1 - E_2}{R_1 + R_2} \right) R_1 - E_1$$

$$\Delta\phi = -4V$$

3.18)

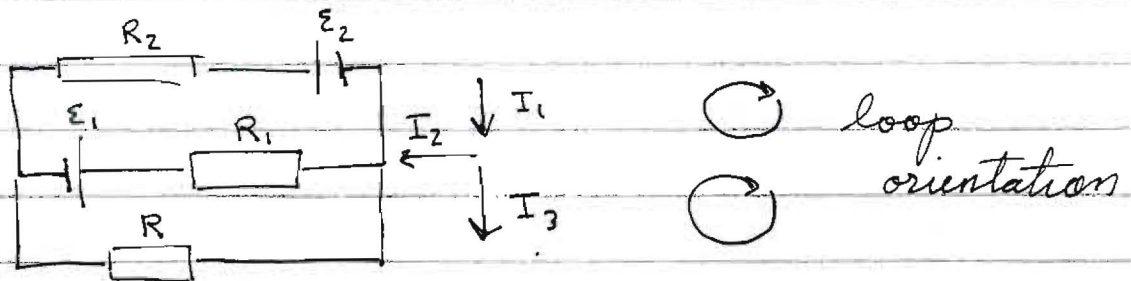

$$\textcircled{1} \quad -I_1 R_2 + \varepsilon_2 - I_2 R_1 + \varepsilon_1 = 0$$

$$\textcircled{2} \quad -I_2 R_1 + \varepsilon_1 + I_3 R = 0$$

$$\textcircled{3} \quad I_1 = I_3 + I_4$$

$$\textcircled{3} \rightarrow \textcircled{1} \quad -I_2 R_2 - I_3 R_2 + \varepsilon_2 - I_2 R_1 + \varepsilon_1 = 0 \quad \textcircled{4}$$

$$-I_2 R_1 + \varepsilon_1 + I_3 R = 0$$

From second equation  $I_2 = \frac{R I_3 + \varepsilon_1}{R_1}$  put that into  $\textcircled{4}$ , solve for  $I_3$

$$-\frac{R_2}{R_1} \varepsilon_1 + \varepsilon_2 = \left( \frac{R_2 R}{R_1} + R_2 + R \right) I_3$$

$$I_3 = \frac{\varepsilon_2 R_1 - \varepsilon_1 R_2}{R_2 R + R_2 R_1 + R_1 R}$$

$$I_3 = 0.02 \text{ A}$$

$$\varepsilon_1 = 1.5$$

$$\varepsilon_2 = 3.7$$

$$R_1 = 10$$

$$R_2 = 20$$

$$R = 5$$